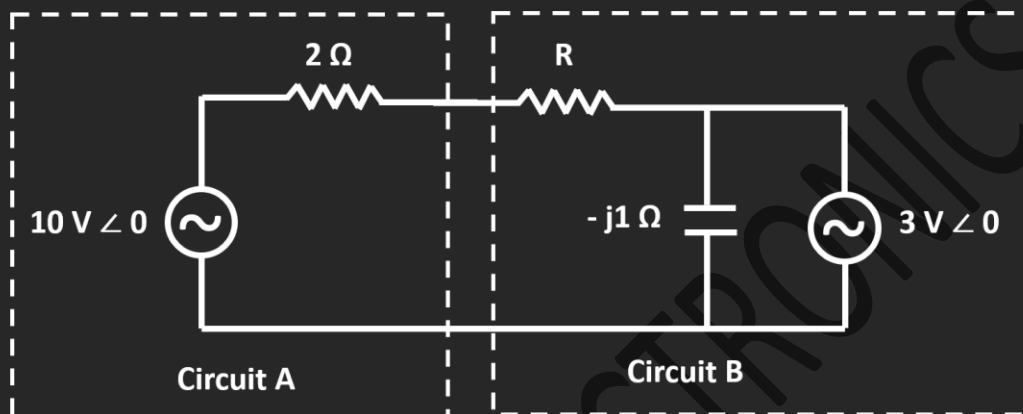


## Quiz#261

For the given circuit, assume that both voltage sources are in a phase. The value of  $R$  for which the maximum power will be transferred from the circuit A to B is



- A)  $0.8\ \Omega$
- B)  $1.4\ \Omega$
- C)  $2\ \Omega$
- D)  $2.8\ \Omega$

**Answer:** <https://youtu.be/q9xdgPQ5mgQ>

## Quiz#105

For the network shown, Thevenin's equivalent voltage source and resistance are,




- A)  $1\text{ mV}$  and  $10\ \Omega$
- B)  $1\text{ V}$  and  $1\text{ k}\Omega$
- C)  $1\text{ mV}$  and  $1\text{ k}\Omega$
- D)  $1\text{ V}$  and  $10\ \Omega$

**Answer:** <https://youtu.be/8TZyFMuGE6U>
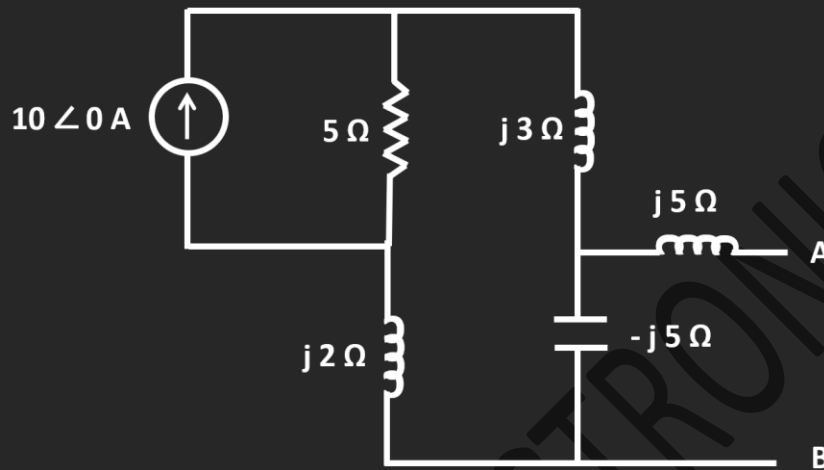
### Quiz#242

The Norton's equivalent current through terminal AB is \_\_\_\_\_



Answer: <https://youtu.be/Vzd2S7x2mrM>

### Quiz#233

The voltage current relationship feeding the network N is shown in the figure. The Norton's equivalent of the network N will have  $I_N$  and  $R_N$  as



A) 5 A and 25 Ω

C) 5 A and 5 Ω

B) - 5 A and 5 Ω

D) - 5 A and - 5 Ω

Answer: <https://youtu.be/o5Um42EbTZ8>

### Quiz#230

A voltage source delivers 4 A to the load when load is  $5 \Omega$  and 2 A when the load is  $20 \Omega$ . The maximum power which can be delivered by the source is

A) 40 W

C) 90 W


B) 80 W

D) 100 W

Answer: <https://youtu.be/6lmf6fHEBjA>
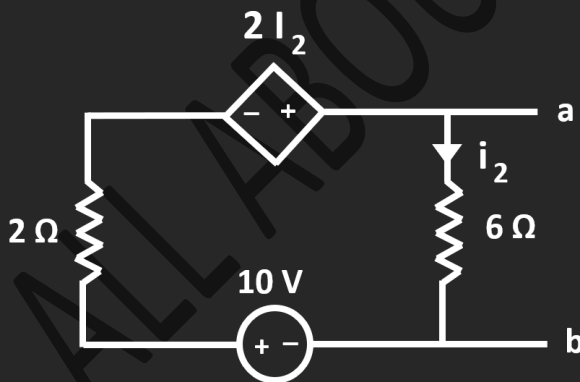
### Quiz#228

For the given circuit, the Thevenin's equivalent resistance across the terminal ab is



A)  $1 \Omega$

B)  $2 \Omega$


C)  $3 \Omega$

D)  $4 \Omega$

Answer: <https://youtu.be/V5glnRtiOjw>
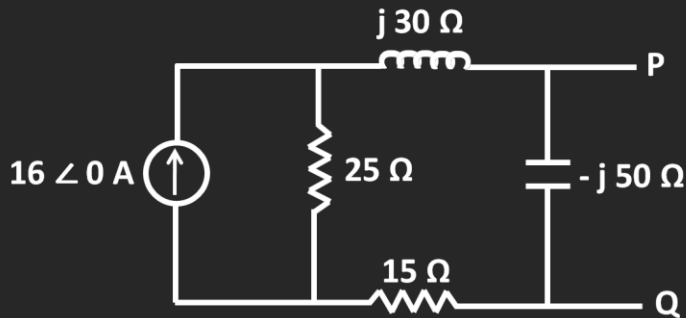
### Quiz#145

For the given circuit, the Norton's equivalent current (in amperes) with respect to terminals P and Q is



A)  $6.4 - j 4.8$

B)  $6.56 - j 7.87$

C)  $10 + j 0$

D)  $16 + j 0$

Answer: <https://youtu.be/mOtL1jzyzlw>

### Quiz#196

For the maximum power transfer between the two cascaded sections of the electrical network, the relationship between the output impedance  $Z_1$  of the first section to the input impedance  $Z_2$  of the second section is

A)  $Z_2 = Z_1$

C)  $Z_2 = Z_1^*$


B)  $Z_2 = -Z_1$

D)  $Z_2 = -Z_1^*$

Answer: <https://youtu.be/95Fgx64zybc>
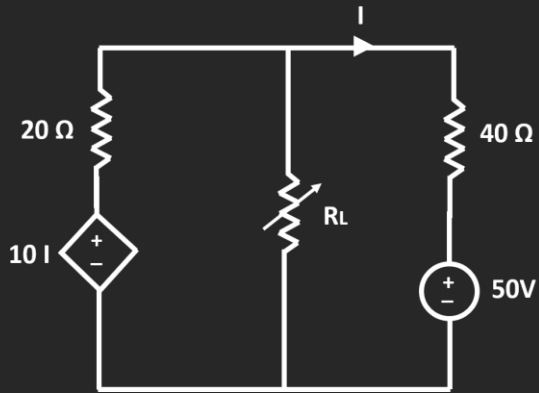
## Quiz#169

For the given circuit, find the value of load resistor  $R_L$  for the maximum power transfer. And also calculate the maximum power.



- A)  $R_L = 20\ \Omega$  and  $P_{\max} = 1.25\ \text{W}$
- B)  $R_L = 16\ \Omega$  and  $P_{\max} = 1.56\ \text{W}$
- C)  $R_L = 20\ \Omega$  and  $P_{\max} = 31.25\ \text{W}$
- D)  $R_L = 40\ \Omega$  and  $P_{\max} = 15.6\ \text{W}$

**Answer:** <https://youtu.be/Av1ec2LTqKk>

ALL ABOUT ELECTRONICS