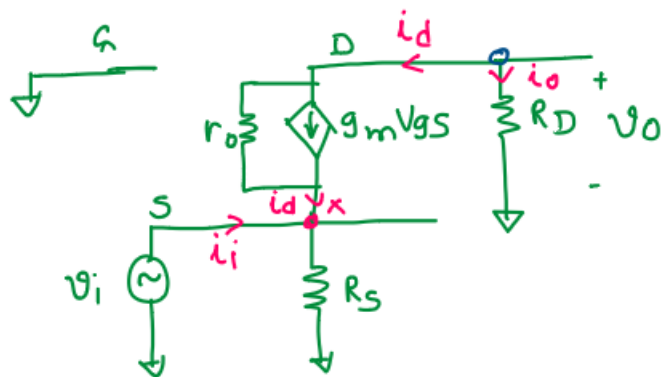


For Small signal Analysis, equivalent circuit



Voltage gain and input impedance

Applying KCL at node X,

$$i_i - \frac{v_i}{R_S} + i_D = 0 \dots (1)$$

$$i_d = g_m v_{gs} + \frac{v_o - v_i}{r_o} \quad \text{--- (2)}$$

Applying KCL at output node

$$i_o + i_d = 0$$

$$\Rightarrow i_d = -\frac{v_o}{R_D} \quad \text{--- (3)} \quad \left(\because i_o = \frac{v_o}{R_D} \right)$$

Equating eqⁿ (2) & (3) -

$$g_m v_{gs} + \frac{v_o - v_i}{r_o} = -\frac{v_o}{R_D}$$

$$\text{Also, } v_{gs} = -v_i$$

$$\Rightarrow g_m v_i + \frac{v_i}{r_o} = \frac{v_o}{R_D} + \frac{v_o}{r_o}$$

$$\Rightarrow v_i \left[g_m + \frac{1}{r_o} \right] = v_o \left[\frac{1}{R_D} + \frac{1}{r_o} \right]$$

$$1 \Rightarrow \frac{V_0}{V_i} = A_0 = \frac{g_m + \frac{1}{r_o}}{\frac{1}{R_D} + \frac{1}{r_o}} \quad \dots (4)$$

If $r_o = \infty$, then $A_0 = g_m R_D$

Now, equating eqⁿ (1) & (3)

$$i_i - \frac{V_i}{R_S} = \frac{V_0}{R_D}$$

$$\Rightarrow i_i - \frac{V_i}{R_S} = \frac{A_0 \times V_i}{R_D}$$

$$\Rightarrow i_i - \frac{V_i}{R_S} = \frac{V_i}{R_D} \left[\frac{g_m + \frac{1}{r_o}}{\frac{1}{R_D} + \frac{1}{r_o}} \right]$$

$$\Rightarrow i_i - \frac{V_i}{R_S} = V_i \left[\frac{g_m + \frac{1}{r_o}}{1 + \frac{R_D}{r_o}} \right]$$

$$\Rightarrow i_i = v_i \left[\frac{g_m + \frac{1}{r_o}}{1 + \frac{R_D}{r_o}} + \frac{1}{R_S} \right]$$


$$\Rightarrow \frac{i_i}{v_i} = \frac{g_m + \frac{1}{r_o}}{1 + \frac{R_D}{r_o}} + \frac{1}{R_S}$$

$$\Rightarrow \frac{1}{z_i} = \frac{g_m r_o + 1}{r_o + R_D} + \frac{1}{R_S}$$

$$\Rightarrow z_i = \frac{r_o + R_D}{1 + g_m r_o} \parallel R_S$$


$$\text{If } r_o = \infty \Rightarrow z_i = \frac{1}{g_m} \parallel R_S$$

Output Impedance:

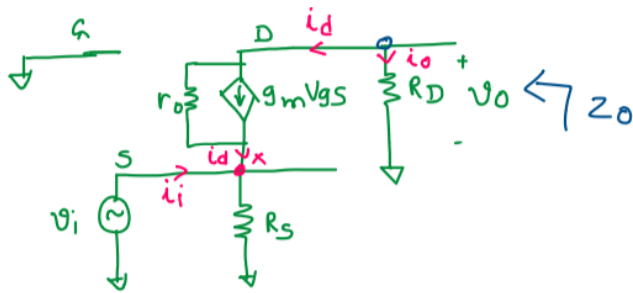

For output impedance, let's consider all the independent sources as zero.

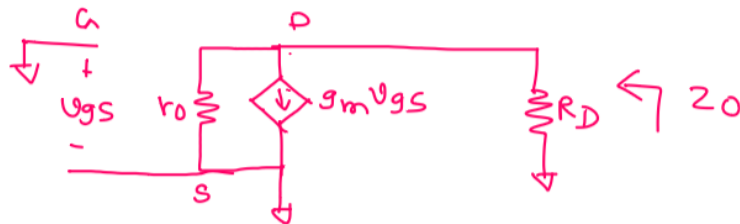\Rightarrow considering $v_{in}=0$, R_S will get short circuited.



Since, $V_{GS} = 0$, dependent current source will also be zero

And $Z_0 = r_o \parallel R_D$

That means for CG amplifier,

$$Z_0 = r_o \parallel R_D$$

$$Z_i = R_S \parallel \left[\frac{r_o + R_D}{1 + g_m r_o} \right]$$

$$A_v = \left[\frac{g_m + \frac{1}{r_o}}{\frac{1}{R_D} + \frac{1}{r_o}} \right]$$